

Roll No. \_\_\_\_\_

Total No. of Pages : 02

Total No. of Questions : 18

**B.Tech. (CSE/IT) (2018 Batch) (Sem.-3)**

**DIGITAL ELECTRONICS**

**Subject Code : BTES-301-18**

**M.Code : 76435**

**Time : 3 Hrs.**

**Max. Marks : 60**

**INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

**SECTION-A**

**Write briefly :**

1. Perform the subtraction  $1001_2 - 1110_2$  using 1's complement method of subtraction.
2. Convert  $38_{16}$  hexadecimal number to binary.
3. Convert the BCD number 00011000 to decimal number.
4. Write the truth table of 3-input OR gate.
5. Give the functional difference between a NAND gate and a negative OR gate.
6. Construct a truth table for the given Boolean expression  $AB+BC$ .
7. Give the comparison between synchronous & Asynchronous sequential circuits.
8. Determine the resolution of the output from a DAC that has a 12-bit input.
9. What is the difference between static RAM and dynamic RAM?
10. Draw the logic diagram for SR latch using two NOR gates.

### SECTION-B

11. Using the Boolean Algebra, simplify the expression:

$$(A + \overline{A})(AB + ABC)$$

12. Use a Karnaugh map to simplify the function to its minimum sum of product form:

$$X = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + \overline{A}BCD$$

13. Design a Excess-3 to BCD code converter using minimum number of NAND gates.
14. Explain the operation of master-slave J-K flip flop. Give its advantages.
15. Design a 4-bit asynchronous up/down counter and explain its working with the help of timing diagram.

### SECTION-C

16. Simplify using K-map

$$f(ABCD) = \Pi M(1,3,5,7,8,9,10,13,15) \text{ and implement using NAND/NOR logic.}$$

17. a) Explain how a 4-bit R/2R register DAC works?
- b) Design and working of a synchronous MOD- 6 counter using JK FF.
18. Write short notes on **any two** :
- a) PLA
- b) Ring Counter
- c) BCD to 7 segment decoder

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**

Roll No.

Total No. of Pages : 02

Total No. of Questions : 18

**B.Tech.(CSE/IT) (2018 Batch) (Sem.-3)**

**DIGITAL ELECTRONICS**

**Subject Code : BTES-301-18**

**M.Code : 76435**

**Time : 3 Hrs.**

**Max. Marks : 60**

**INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A is COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

**SECTION-A**

**Write briefly :**

- 1) What are the universal gates? Justify.
- 2) State De-Morgan's Theorem.
- 3) Write the characteristic equation of  $4 \times 1$  multiplexer.
- 4) State the differences between combinational and sequential circuits.
- 5) Draw the excitation table of D flip flop.
- 6) Convert 101011 into Decimal system & Octal system.
- 7) Draw the state diagram of 3 bit up counter.
- 8) State the functions of flip flops.
- 9) Define Melay machine with state diagram.
- 10) Compare PLA, PAE and PROM.

### SECTION-B

- 11) Design a  $5 \times 32$  decoder using  $3 \times 8$  decoder and summarize that how many decoders are required for designing?
- 12) Design a two bit magnitude comparator and draw its logic circuit.
- 13) Elucidate the design procedure of synchronous sequential circuits.
- 14) Perform the following addition by 2's complement :
  - a) 20 to -26
  - b) 25 to -15.
- 15) What are various laws for Boolean logic simplification?

### SECTION-C

- 16) Design and implement BCD to gray code converter using PAL.
- 17) a) What are the different logic gates? Give their truth tables.  
b) Write a short note on static, bipolar and MOSFET RAM cell.
- 18) Draw the logic circuit, excitation table & truth table of RS Flip-Flop.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**